

Αδ. 7.96

500 σπείρες. (K)

$$L = 0,2 \text{ H}$$


$$R_1 = 30 \Omega$$

$$R_2 = 60 \Omega$$


$$R_3 = 30 \Omega$$

$$E = 120 \text{ V}$$

$$r = 10 \Omega$$

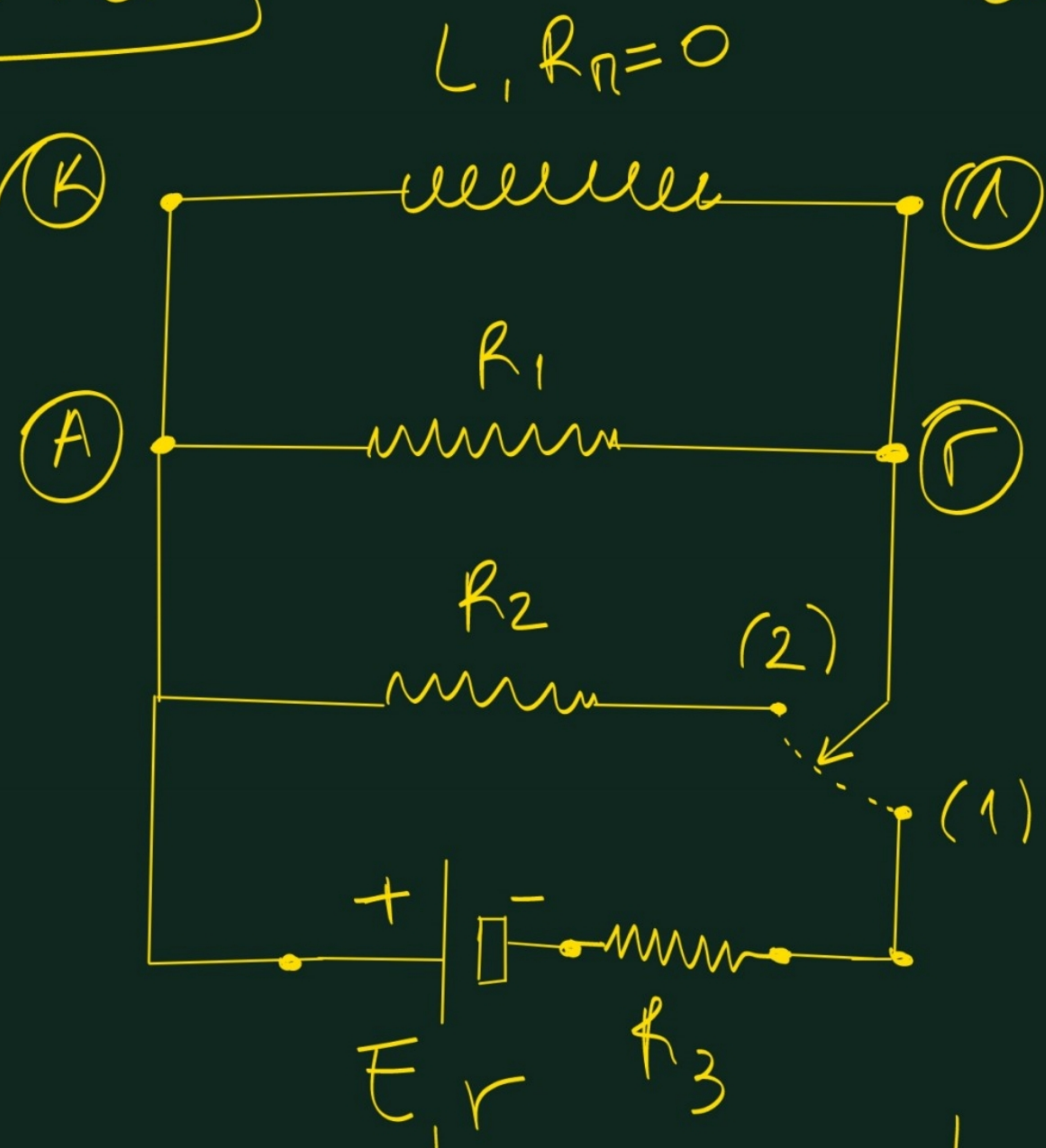

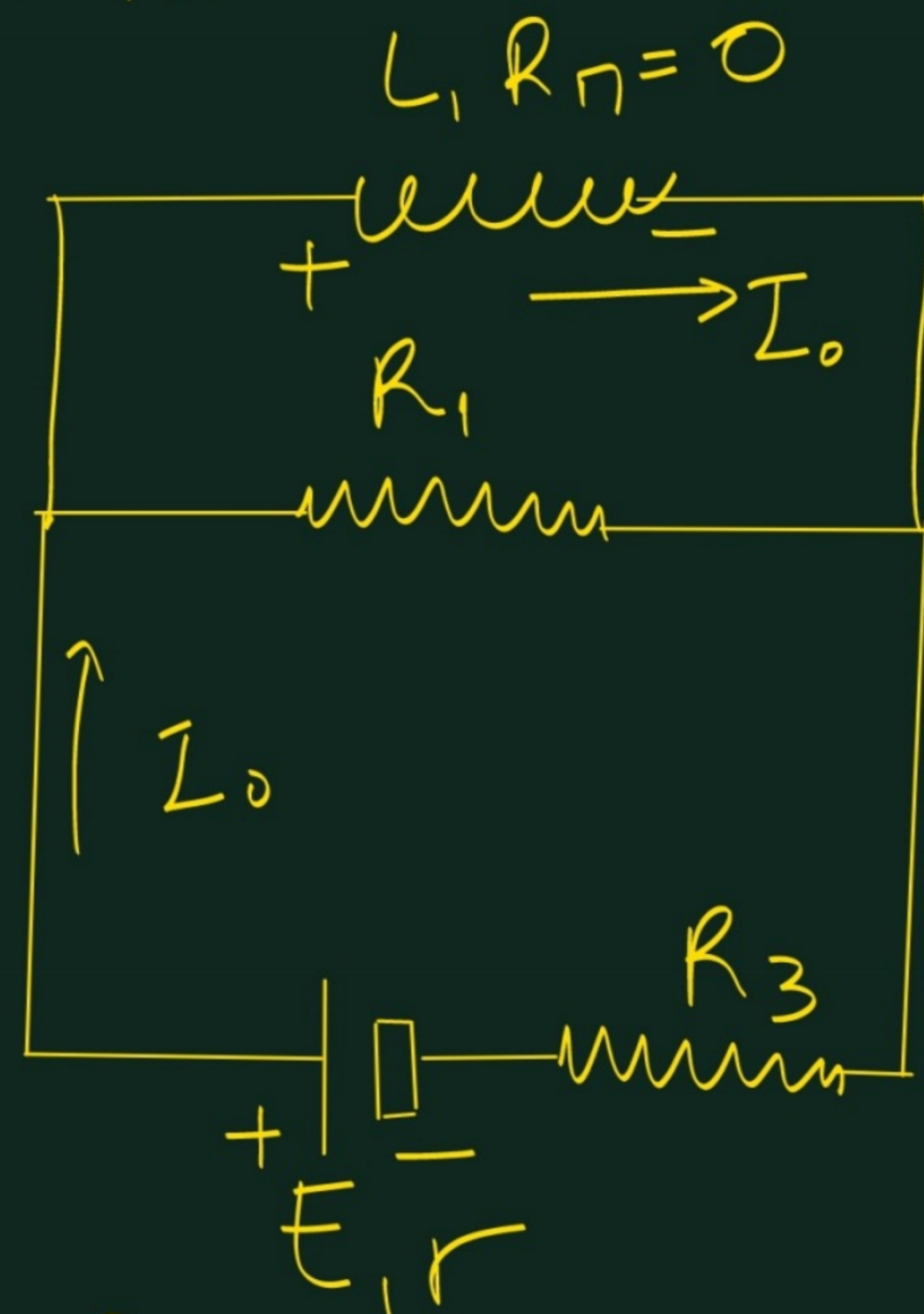α) Με το υστέρησέ στη θέση (1)
έχουμε το κύκλωμα:



Στη θέση
απόρριβη το
πηνίο συμπεριφέρεται
σαν βραχυκύκλωμα.

$$I_0 = \frac{E}{R_3 + r} =$$

$$I_0 = \frac{120}{40} = 3 \text{ A}$$

$$L = \mu_0 \mu \frac{N^2}{\ell} A$$

$$\Phi_{\max} = BA = \mu \mu_0 n \bar{I}_0 A = \mu \mu_0 \frac{N}{\ell} \cdot A \cdot \bar{I}_0 = \frac{L \bar{I}_0}{N}$$

$$\text{Αρα: } \Phi_{\max} = \frac{LI_0}{N} = \frac{0,2 \cdot 3}{500} \Rightarrow$$


$$\Phi_{\max} = \frac{0,6}{5 \cdot 10^2} = \frac{6 \cdot 10^{-1}}{5 \cdot 10^2} \Rightarrow$$

$$\Phi_{\max} = 1,2 \cdot 10^{-3} \text{ Wb.}$$

$$L, R_n = 0$$

β) i)

Μεταγωγός
6cm
Θέση (2)

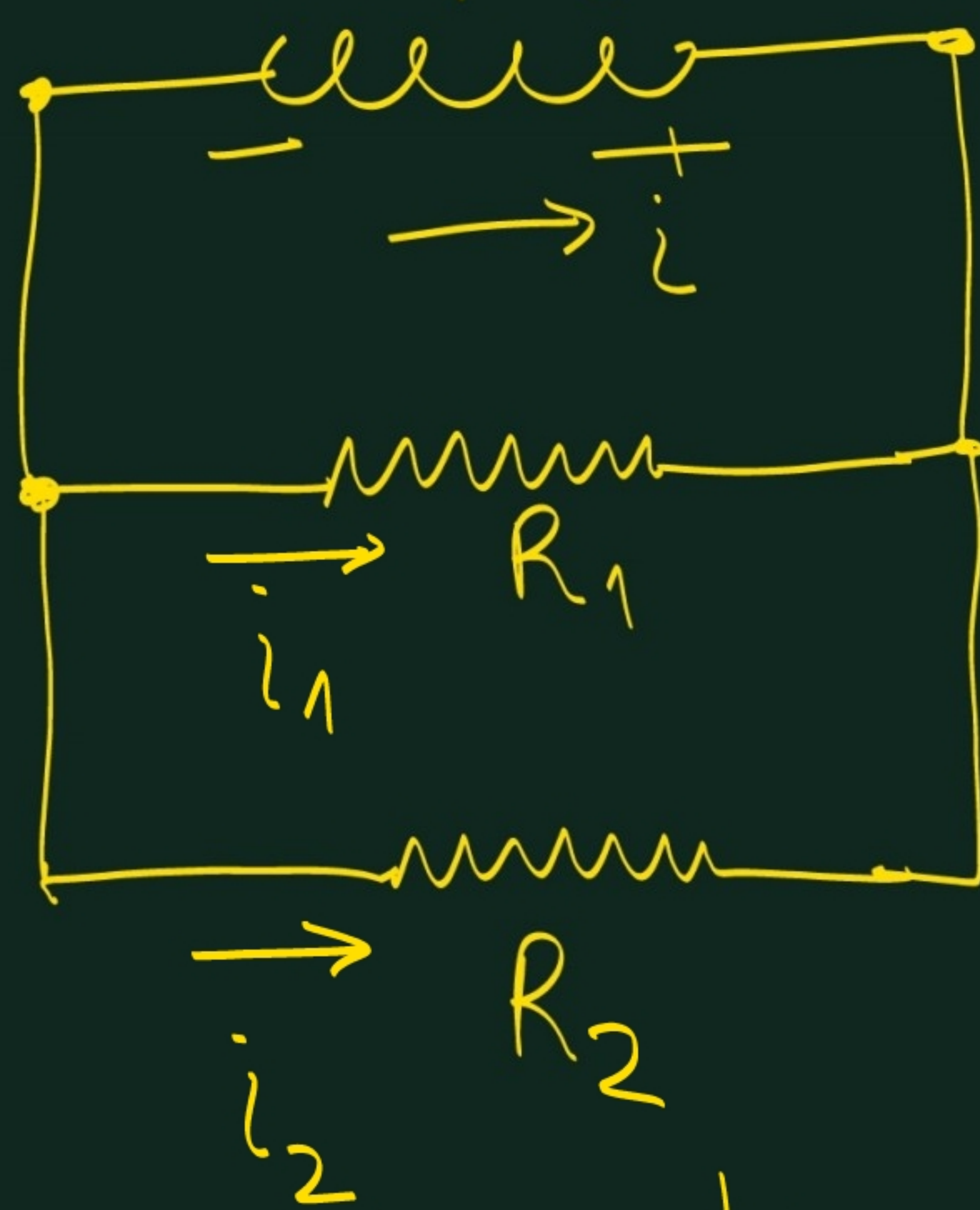

$$\mathcal{E}_{\text{ωρ}} = i R_{1,2} \Rightarrow$$

$$-L \frac{\Delta i}{\Delta t} = i \frac{R_1 R_2}{R_1 + R_2} \Rightarrow$$

$$L \frac{\Delta i}{\Delta t} = -i \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{Αν } i = \frac{I_0}{2} \text{ έχουμε:}$$

$$V_L = L \frac{\Delta i}{\Delta t} = |\mathcal{E}_{\text{ωρ}}| = \frac{I_0}{2} \frac{R_1 R_2}{R_1 + R_2} = \frac{3}{2} \cdot \frac{30 \cdot 60}{30 + 60}$$

$$= \frac{3}{2} \cdot \frac{1800}{90} = \frac{3}{2} \cdot 20 = 30 \text{ Volt}$$

$$|\mathcal{E}_{\text{ωρ}}| = \frac{|\Delta \Phi|}{\Delta t} \text{ για όλες τις σπείρες. Αρα για μία σπείρα:}$$

$$\frac{|\Delta \Phi_{\text{πέρας}}|}{\Delta t} = \frac{1}{N} \frac{|\Delta \Phi|}{\Delta t} =$$

$$= \frac{1}{N} \cdot |E_{\text{αωτ}}| = \frac{1}{500} \cdot 30 =$$

$$= \frac{0,6}{100} = 6 \cdot 10^{-3} \text{ Wb/sec (Volt)}$$

ii) Πρέπει να βρούμε τη σταγιάα ισχύ του αντιστάτη R_1 .

$$P_1 = i_1^2 R_1 = \frac{\Delta Q_{R_1}}{\Delta t}$$

$$L \cdot \frac{\Delta i}{\Delta t} = -i \frac{R_1 R_2}{R_1 + R_2}$$

$$i = i_1 + i_2.$$

$$i_1 R_1 = i_2 R_2$$

$$i = \frac{I_0}{2}$$

$$i_1 \cdot 30 = i_2 \cdot 60 \Rightarrow$$

$$\Rightarrow i_1 = 2i_2 \Rightarrow i_2 = \frac{i_1}{2}$$

$$i = i_1 + \frac{i_1}{2} \Rightarrow i = \frac{3i_1}{2} \Rightarrow$$

$$\frac{I_0}{2} = \frac{3}{2} i_1 \Rightarrow \frac{3}{2} = \frac{3}{2} \cdot i_1 \Rightarrow i_1 = 1 \text{ A}$$

$$\text{Άρα: } \frac{\Delta Q_{R_1}}{\Delta t} = 1^2 \cdot 30 = 30 \text{ Watt}$$

$$8) U_L = \frac{1}{2} L i^2$$

$$\frac{\Delta U_L}{\Delta t} = L i \frac{\Delta i}{\Delta t} = i U_L$$

$$U_L = Q_{R_1} + Q_{R_2} \Rightarrow$$

$$\frac{\Delta U_L}{\Delta t} = \frac{\Delta Q_{R_1}}{\Delta t} + \frac{\Delta Q_{R_2}}{\Delta t} =$$

$$= i_1^2 R_1 + i_2^2 R_2$$

$$\frac{\Delta Q_{R_2}}{\Delta U_L} = \frac{1}{3} \Rightarrow \Delta U_L = 3 \Delta Q_{R_2}$$

$$i_1 R_1 = i_2 R_2 \Rightarrow 30 i = 60 i_2 \Rightarrow i_1 = 2 i_2$$

$$\begin{aligned} \frac{\Delta Q_{R_2}}{\Delta t} &= \frac{i_2^2 R_2}{i_1^2 R_1 + i_2^2 R_2} \Rightarrow \frac{\Delta Q_{R_2}}{\Delta U_L} = \frac{i_2^2 R_2}{4 i_2^2 R_1 + i_2^2 R_2} = \\ &= \frac{R_2}{4 R_1 + R_2} = \frac{60}{4 \cdot 30 + 60} = \frac{60}{180} = \\ &= \frac{1}{3} \end{aligned}$$

$$\sum \Delta U_L = 3 \sum \Delta Q_{R_2} \Rightarrow$$

$$U_{L, \text{apx}} = 3 Q_{R_2, 0,1} \Rightarrow \frac{1}{2} L I_0^2 = 3 Q_{R_2, 0,1} \Rightarrow \frac{1}{2} \cdot 0,2 \cdot 3^2 = 3 Q_{R_2, 0,1} \Rightarrow$$

$$Q_{R_2, 0,1} = 0,3 \text{ Joule.}$$

